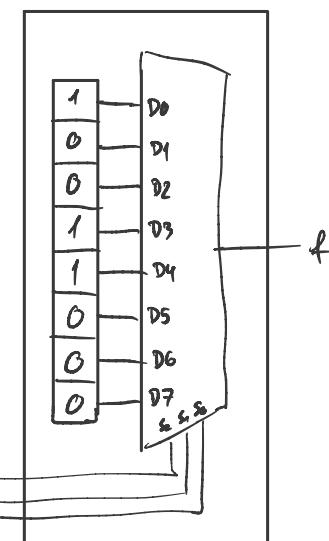


5. ZADACA

- ① CLB ostvarjen pomoću LUT s 3 ul.
- Realiziraj f kao produkt mesta

$$f(A, B, C) = \underbrace{M(1, 2, 5, 6, 7)}_{\text{ovo su nule}}$$


A	B	C	f
0	0	0	1
1	0	0	0
2	0	1	0
0	1	1	1
1	0	0	1
5	1	0	1
6	1	1	0
7	1	1	0



- ② CLB ostvarjen uporabom LUT s 3 celice
- Realiziraj fju:


$$f(A, B, C) = ((B \text{ AND } B) \text{ AND } C) = (B \cdot B) \cdot C = BC$$

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

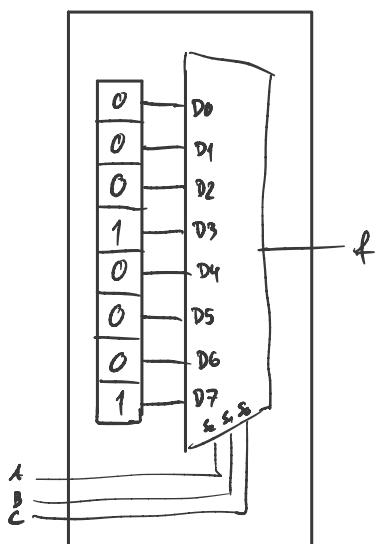

- ③ Programirati 4-uklanjivi LUT s D-bistabilom tabo da se


A	B	C	Q _{n+1}
0	0	0	1
0	0	1	Q _n
0	1	0	Q _n
0	1	1	Q _n
1	0	0	0
1	0	1	Q _n
1	1	0	Q _n
1	1	1	0

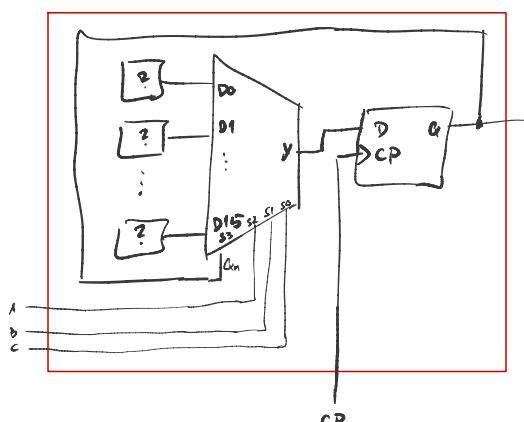

Q _n	A	B	C	Q _{n+1}
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0


(4)

A_n	B_n	C_n	D_n	A_{in}	B_{in}	C_{in}	D_{in}	S_{1n}
0	0	0	0	1	0	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	0	0	0	1	0	2
0	0	1	1	0	0	0	1	3
0	1	0	0	1	0	1	0	4
0	1	0	1	1	0	1	0	5
0	1	1	0	0	1	1	0	6
0	1	1	1	0	0	1	0	7
1	0	0	0	0	1	0	0	8
1	0	0	1	0	1	0	0	9
1	0	1	0	1	1	0	1	10
1	0	1	1	1	1	0	1	11
1	1	0	0	1	1	0	1	12
1	1	0	1	1	1	0	1	13
1	1	1	0	1	1	1	1	14
1	1	1	1	0	1	1	1	15

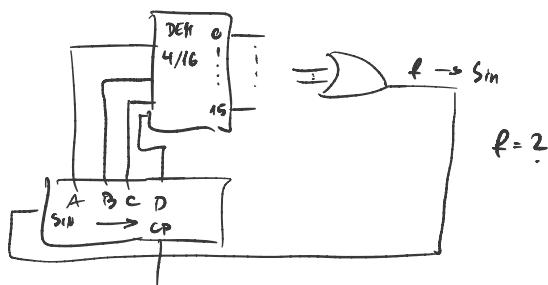

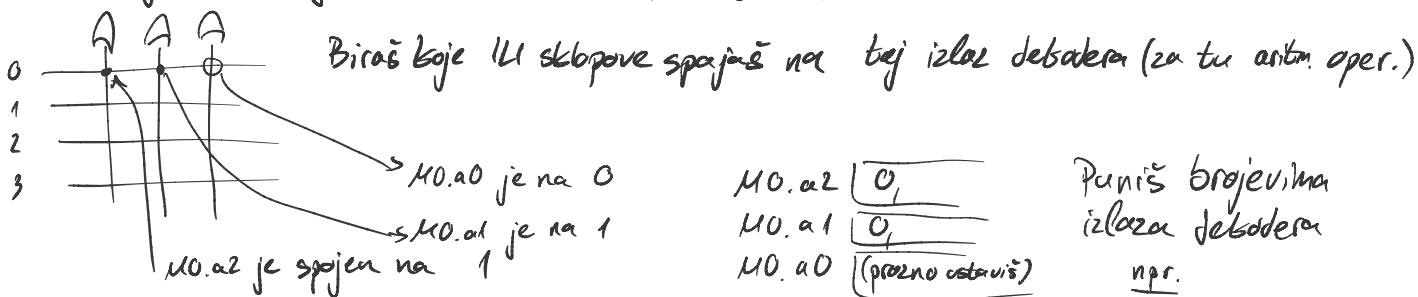(5) WTF? Neću to pisať.

X, X, X bitaju operacijy. Kad odaberem operaciju npr. 0, 1, 2 ili 3 tamo bude log. „1“.



(6) 3-bitni pretvornik sa sekvensnom aproksimacijom

$$U_{ULF} = 11.4V$$

$$t_1 = 77\text{ms}$$

$$U_{UL2} = 5.6V$$

$$t_2 = ?$$

$$t \neq f(U)$$

$$t \text{ ostaje isto}$$

$$P_f: 77\text{ms}$$

$$MO.a2 \boxed{0, 1, 2}$$

$$a^1 \boxed{1, 2}$$

$$a^0 \boxed{3}$$

(7)

Q_1''	Q_1'''	Q_2''	Q_2'''	Q_3''	Q_3'''
0	0	0	1	0	0
0	0	1	0	1	1
0	1	0	1	0	1
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

$(6, 7, 1, 3, 0, 4, 2, 5, 6)$

⑥

Q_3^n	Q_2^n	Q_1^n	Q_0^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}	S2	R2	S1	R1	S0	R0
0	0	0	1	1	0	1	0	0	X	1	0	0	0
0	0	1	0	1	1	0	X	1	0	X	0	1	1
0	1	0	1	1	0	1	0	X	0	0	X	2	1
0	1	1	0	0	0	0	X	0	1	0	1	3	1
1	0	0	1	1	1	X	0	1	0	1	0	4	0
1	0	1	0	1	0	0	1	1	0	0	1	5	1
1	1	0	1	0	0	X	0	0	1	0	X	6	0
1	1	1	0	0	1	0	1	0	1	X	0	7	1

Q_3^n	Q_2^n	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

⑦

D	Q_3^n	Q_2^n	Q_1^n	Q_0^n	Q_3^{n+1}	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
0	0	0	0	0	0	0	1	0
1	0	0	0	1	0	0	1	1
2	0	0	0	1	0	0	1	0
3	0	0	0	1	1	0	0	1
4	0	0	1	0	0	1	1	0
5	0	0	1	0	1	1	1	1
6	0	0	1	1	0	1	0	0
7	0	0	1	1	1	0	0	1
8	0	1	0	0	1	0	1	0
9	0	1	0	0	1	0	1	1
10	0	1	0	1	0	1	1	0
11	0	1	0	1	1	1	0	1
12	0	1	1	0	0	1	1	0
13	0	1	1	0	1	1	1	1
14	0	1	1	1	0	0	0	0
15	0	1	1	1	1	0	0	1
16	1	0	0	0	1	1	0	1
17	1	0	0	0	1	1	1	0
18	1	0	0	1	0	1	1	1
19	1	0	0	1	1	0	0	0
20	1	0	1	0	0	0	0	1
21	1	0	1	0	0	0	1	0
22	1	0	1	1	0	0	1	1
23	1	0	1	1	1	0	1	0
24	1	1	0	0	0	1	0	1
25	1	1	0	0	1	0	1	0
26	1	1	0	1	0	1	1	1
27	1	1	0	1	1	0	0	0
28	1	1	1	0	0	1	0	1
29	1	1	1	0	1	0	1	0
30	1	1	1	1	0	1	0	1
31	1	1	1	1	1	1	0	0

C=1 X X X X X 0 0 0 0

(12)

potrebna pobudica

trenutno s.		sljedeće					
Q_3''	Q_2''	Q_1'''	Q_0'''	D_1	D_2	D_3	D_2
0	0	0	1	0	1	0	0
0	1	1	0	1	0	0	1
1	0	1	1	1	1	1	1
1	1	0	0	0	1	1	1

\downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow

L_1 L_2 L_3 L_4 L_5 L_6

$s=1$ $s=0$

BISTABIL KOMB. SKLOPOVI

(9)

$$B: 6 \rightarrow 8 \rightarrow 13 \rightarrow 4 \rightarrow 5 \rightarrow 3 \rightarrow 14 \rightarrow 10 \rightarrow 2 \rightarrow 7 \rightarrow 12 \rightarrow 15 \rightarrow 9 \rightarrow 0 \rightarrow 1 \rightarrow 11$$

$$ROM: 0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 4 \rightarrow 5 \rightarrow 6 \rightarrow 7 \rightarrow 8 \rightarrow 9 \rightarrow A \rightarrow B \rightarrow C \rightarrow D \rightarrow E \rightarrow F$$

B	ROM
0	D
1	E
2	8
3	5
4	3
5	4
6	0
7	9
8	1
9	C
10	7
11	F
12	A
13	2
14	6
15	B

(10)

Zadani ciklus:

1, 4, 13, 12, 7, 0, 15, 11, 2, 9, 8, 6, 3, 5, 10, 14

bita MUX

 $\rightarrow 0 = R_1$ $\rightarrow 1 = R_2$

bita mem. odabiraju

registra

	Q_3''	Q_2''	Q_1'''	Q_0'''	D
R1	0	0	0	0	F
	0	0	0	1	4
	0	0	1	0	9
	0	0	1	1	5
	0	1	0	0	D
	0	1	0	1	A
	0	1	1	0	3
	0	1	1	1	0
	1	0	0	0	6
	1	0	0	1	8
	1	0	1	0	E
R2	1	0	1	1	2
	1	1	0	0	7
	1	1	0	1	C
	1	1	1	0	1
	1	1	1	1	B

12, 15, 7, 11, 13, 2, 10, 3, 8, 9, 5, 14, 0, 4, 1, 6

	Q_3''	Q_2''	Q_1'''	Q_0'''	D
R1	0	0	0	0	4
	0	0	0	1	6
	0	0	1	0	A
	0	0	1	1	8
	0	1	0	0	1
	0	1	0	1	E
	0	1	1	0	C
	0	1	1	1	B
	1	0	0	0	9
	1	0	0	1	5
	1	0	1	0	3
	1	0	1	1	D
	1	1	0	0	F
	1	1	0	1	2
	1	1	1	0	0
	1	1	1	1	7