

DIGITALNA LOGIKA

GLAVNIĆ
VLADO

JAKOV
JAKOVAC

- Brojčani sustavi i kodovi

- pohranjivanje brojeva u registrima
 - ograničen broj mjesto
 - $B^n = m$: modul
 - $W = B^n - 1$ i najveći n-znamenkasti broj
- komplementi broja
 - konisti pretvaranje oduzimanja u zbrojovanje
 - mogućnost koristenja istog hardware-a za zbrojovanje i oduzimanje

$$21) R_1 = 0A7E3FF8$$

$$R_2 = 0004FF2A$$

$$R_3 = R_2 - R_1 = ?$$

$$\bar{R}_1 = F581C007$$

$$\bar{R}_1 = F581C008$$

$$\begin{array}{r} R_3 = 0004FF2A \\ + F581C008 \\ \hline F586BF32 \end{array}$$

• binarno kodiranje/dekodiranje

- izražavanje simbola/znakova u binarnom obliku
- prikaz simbola unutar digitalnog sustava
- zaštita od djelovanja pogrešaka prilikom prenoса ili pohrane podataka

• prikaz dekadskih znamenki

~ dekadski kodovi (npr. BCD, 2421, XS-3, bitvinski)

$$22) 0111 \quad 1000 \quad 0010 \quad 0101$$

$$+ \quad 8 \quad 2 \quad 5$$

$$N_{10} = 2174$$

$$+ \quad 1$$

$$\bar{N}_{10} = 2175$$

$$2175 = 0010 \quad 0001 \quad 0111 \quad 0101$$

- Zaštitno kodiranje

- otkrivanje i ispravljanje pogrešaka prilikom prenoса ili pohrane podataka
- kodne riječi su moraju razlikovati u više od 1 bita: $d_{min} > 1$
- mora postojati zaliht(fredundancija) R
 - (izvornim kodnim riječima) dodati zaštitne bitove
- otkrivanje pogrešaka ($d_{min}-1$)
- ispravljanje pogrešaka ($(d_{min}-1)/\text{kodnih riječi}$)

$$z_3) 0 \rightarrow 0000000$$

$$1 \rightarrow 1111111$$

$$X=2 = \{0, 1\} \rightarrow \text{kodne riječi}$$

$$d_{min} = 7 = 1$$

$$Y = 7 - 1 = 6 \rightarrow \text{otkriva}$$

$$Z = Y/X = 6/2 = 3 \rightarrow \text{ispravlja}$$

• paritet (najjednostavniji način zaštite)

- dodati paritetni bit (VRC)

- otkrivanje neparnih pogrešaka

- višestruko pariranje

• Hammingov kod (n-duljina kodne riječi, k-broj

informacijskih bitova, r-broj zaštitnih bitova)

$$2^r \geq k+r+1, \quad n = k+r$$

k	r	n
1	2	3
4	3	7
11	4	15
120	7	127

$$25) R_p = \frac{1}{7+1} = \frac{1}{8} \quad \frac{R_H}{R_p} = \frac{32}{11} \sim 2.91$$

$$R_H = \frac{4}{7+4} = \frac{4}{11}$$

— Osnove digitalne logike —

- sve funkcije digitalnog sustava temeljene na malom skupu "osnovnih logičkih funkcija"

$$\bar{A} \oplus B \oplus \bar{C} = (\bar{A} \oplus \bar{C}) \oplus B$$

- osnovne logičke funkcije na os. log. sklopovima

$$= A \oplus C \oplus B$$

abstraktni "logičke varijable"

- konstante: $T \sim$ istina; $\perp \sim$ neistina(0)

- kombinacije: ne, i, ili

• Boolean funkcija je izraz koji sadrži varijable

i kombinatore

- tablica kombinacija (2^n broj redaka)

• Boolean algebre

- dvije osnovne operacije: +, ·

- skup aksioma

• Kanonski oblik

$$f(A, B) = (M_0 + M_2)(M_1 + M_3)(M_2 + M_3)$$

A	B	f
0	0	b_0
0	1	b_1
1	0	b_2
1	1	b_3

→ preko nula (maxtermi)

$$\rightarrow M_0 = A+B, M_1 = A+\bar{B}, M_2 = \bar{A}+B, M_3 = \bar{A}+\bar{B}$$

$$f(A, B) = m_0 \cdot \bar{A} \cdot \bar{B} + m_1 \cdot \bar{A} \cdot B + m_2 \cdot A \cdot \bar{B} + m_3 \cdot A \cdot B$$

→ preko jedinica (mintermi)

$$\rightarrow m_0 = \bar{A} \cdot \bar{B}, m_1 = \bar{A} \cdot B, m_2 = A \cdot \bar{B}, m_3 = A \cdot B$$

$$x \oplus y = \sum m(1, 2)$$

$$= \prod M(0, 3)$$

$$T1) a+1=1; a \cdot 0=0 \quad (\text{dominacija})$$

$$f(A, B, C) = \bar{A} + B \cdot \bar{C}$$

$$T2) a+a=a; a \cdot a=a$$

$$= \bar{A}(\bar{B}+B) \cdot (\bar{C}+C) + (\bar{A}+A) \cdot B \cdot \bar{C}$$

$$T3) a=(\bar{a}) \quad (\text{involucija})$$

$$= (\bar{A} \cdot \bar{B} + \bar{A} \cdot B) (\bar{C} + C) + \bar{A} \cdot B \cdot \bar{C} + A \cdot B \cdot \bar{C}$$

$$T4) a+\bar{a} \cdot b=a+b; a \cdot (\bar{a}+b)=a \cdot b$$

$$= \frac{\begin{matrix} 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{matrix}}{ABC} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + ABC$$

$$T5) a+a \cdot b=a;$$

$$= m_0 + m_1 + m_2 + m_3 + m_4$$

$$T6)$$

$$= \sum m(0, 1, 2, 3, 6)$$

$$T7)$$

$$M_{24} = \begin{matrix} 0 & 0 & 0 & 0 & 0 \\ 1 & 1 & 0 & 0 & 0 \end{matrix}$$

$$T8)$$

$$= \bar{A} + \bar{B} + C + B + E$$

$$T9)$$

$$f = A \cdot \bar{B} + C(D+E)$$

$$z1) \overline{x+y} \neq \bar{x} + \bar{y}$$

$$\bar{f} = \overline{A \cdot \bar{B} + C(D+E)} = (\bar{A}+B) \cdot (\bar{C} + \bar{D} \cdot \bar{E})$$

A	B	$A \oplus B$	\bar{A}	\bar{B}	$\bar{A} \oplus \bar{B}$
0	0	0	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

$$= \bar{A} \cdot \bar{B} \cdot \overline{C(D+E)}$$

$$= (\bar{A}+B) \cdot (\bar{C} + \bar{D} + \bar{E})$$

$$25) f(A, B, C, D) = \sum m(1, 2, 3, 7, 11, 15)$$

$$= \prod M(?)$$

$$= \overline{\overline{A} + \overline{B} \cdot \overline{C}}$$

$$= \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} C \overline{D} + \overline{A} \overline{B} \overline{C} D + A \overline{B} C D + A B C D$$

$$= \overline{ABC}$$

$$f_D = (\bar{A} + \bar{B} + \bar{C} + D)(\bar{A} + \bar{B} + C + \bar{D})(A + \bar{B} \bar{C} + D)$$

$$= NI(A, NI(B, NI(C, D)))$$

$$(A + \bar{B} + C + D)(A + B + C + D)$$

$$= M_{14} \cdot M_{13} \cdot M_6 + M_4 \cdot M_0$$

$$= \prod M(0, 4, 6, 13, 14)$$

$$15+0=14+1=13+2=9+6=4+11$$

$$26) f \begin{cases} 2 \text{ min}, 30 \text{ max} \\ \bar{f} \quad 30 \text{ min}, 2 \text{ max} \end{cases}$$

$$27) f = \sum m(3, 5)$$

	A	B	f	$a_1 a_0 b_1 b_0$	
	0	0		0 0 0 0	
A {	1	0		0 0 0 1	
$\frac{a_1}{a_0}$	2	0		0 0 1 0	
$\frac{b_1}{b_0}$	3	0		0 0 1 1	
	0	1		0 1 0 0	m_4
A {	1	1		0 1 0 1	
$\frac{a_1}{a_0}$	2	1		0 1 1 0	
$\frac{b_1}{b_0}$	3	1		0 1 1 1	
	0	0		1 0 0 0	m_8
A {	1	0		1 0 0 1	m_9
$\frac{a_1}{a_0}$	2	0		1 0 1 0	
$\frac{b_1}{b_0}$	3	0		1 0 1 1	
	0	1		1 1 0 0	m_{12}
A {	1	1		1 1 0 1	m_{13}
$\frac{a_1}{a_0}$	2	1		1 1 1 0	
$\frac{b_1}{b_0}$	3	0		1 1 1 1	m_{14}

$$f = \sum m(4, 8, 9, 12, 13, 14)$$

$$28) d_i = \prod M(0, 3, 5, 6)$$

29) NI ; NILI su dualne funkcije

$$\overline{AB} \rightarrow (\overline{A} + \overline{B})$$

* Dualne funkcije su funkcije u kojima se

zamijene 0 i 1 te + i ·.

* NI ; NILI su univerzalne funkcije

$$30) f(A, B, C) = A \cdot (\overline{B} + C)$$

$$= \overline{\overline{A} + (\overline{B} + C)}$$

$$= \overline{\overline{A} + (\overline{\overline{B}} + C)}$$

$$= \overline{\overline{A} + \overline{\overline{B}} + \overline{C}}$$

$$= NIL(NIL(A, A), NIL(NIL(B, B), C))$$

- Minimizacija booleanih izraz

- * Boolean funkcija je opis digitalnog sklopa
 - minimizacija funkcije pojednostavljuje sklop
 - * algebračka minimizacija

BCD-Zahlenmenge = {0, ..., 9}

- * minimační karnaughovina tabulka

$f(A \cup B)$	A	B	f
0	0	0	d_0
d_0	0	1	d_1
d_1	1	0	d_2
d_2	1	1	d_3

$$f = \bar{x}_3 + \bar{x}_2 \cdot \bar{x}_1$$

* nest-pump specificione tablier

- polija s X se interpretiraju kao 1 kada to

pomáž u formovaniu vecíh značkovaní, inaké

se interpretiraju kao D

f(A,B,C)		f(A,B)	
A\B	C	A	B
0	0 0 2 6 4	0 1	0 1
1	1 3 7 5	0 0 1	1 1 3

A mapping diagram between sets A and B.

	1	x	1
1	1	x	1
x	x	1	1
1			1

$$f = \sum m(4,5,13,14,15) + \sum d(1,3,7,8,9)$$

- Razlika susjednih polja su patencije broj 2

$$f(x_1, x_2, x_3, x_4)$$

	18	00	01	11	40
C0	00	0	4	12	8
	01	1	5	13	9*
	10	3	7	15	11
	10	2	6	14	10

74) $f = \sum m(2, 3, 6, 7, 9, 10, 12) + \sum d(0, 1, 14)$

	A\B	00	01	10	11
00	X	1		1	
01	X				
10	1	1	X	1	
11	1	1	X	1	

$$f = \bar{A}C + \bar{C}\bar{D} + \bar{B}\bar{C}D + ABD$$

6xT, 3x TLI

P				
CD	18			
00	00	01	11	10
01		1		1
11	1		1	
10			1	

<u>3</u>	AB				
CD	00	01	02	11	10
	00	1	1	1	1
+	01	1		1	
	01	1	1	1	1
-	10	1	1	1	1

\overline{AB}	-	1	1	1
\overline{CD}	-	1	1	1
	+	1	1	
		1	1	1

$$25) f(A, B, C, D) = \prod M(2, 6; 10, 14) + \prod d(5, 8, 9, 11)$$



f	AB
cD	
	C
	D

* Vremenski hazard

pojavom privremenog impulsa priljubljen premijene stanja ("prijetljivne pojave") izlazi sklop koji može preuzeti funkciju niza.

- statickí 0-hazard (kratkovražný 0)

- statickí 1-hazard (kratkovražný 0)

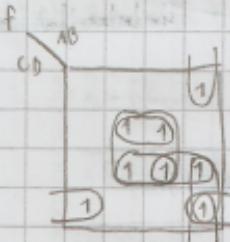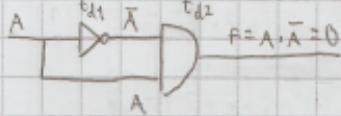

$$a) \# i = \# m + \# p + \# c$$

$$= 8 + 8 + 1$$

$$= 17$$


$$b) \# p_i = 1 + 4$$

$$= 5$$


$$c) \# b_p = 1 + 2$$

$$= 3$$

$$z) f(A, B, C) = \sum m(3, 4, 5, 7)$$

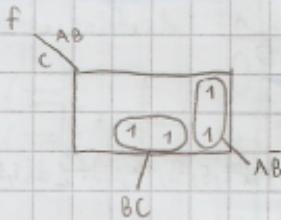

$$f = AB + BC \quad A, C = 1$$

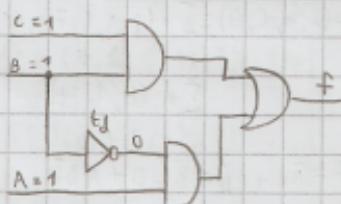


$$B: 0 \rightarrow 1 \quad X$$

$$B: 1 \rightarrow 0 \quad \text{X}$$

$$\begin{matrix} AB \\ 111 \end{matrix} \rightarrow \begin{matrix} AB \\ 101 \end{matrix}$$
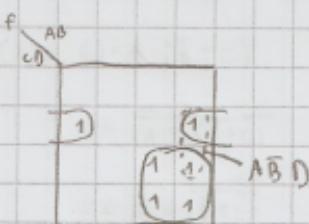
$$z) f(A, B, C, D) = AC + \bar{B}\bar{C}D$$



$$f = AC + \bar{B}\bar{C}D + A\bar{B}D$$

$$z) f(A, B, C, D) = \sum m(2, 5, 7, 8, 10, 11, 13, 15)$$

Boole - Mc Cluskeyova metoda

* postupak v 2 faze

1) Nalaženje potpune sums

2) Nalaženje minimalne sume

- modifikacije za minimiziranje nepotpune specifirane funkcije i višeizlaznih funkcija

* manipuliranje indeksima minterma

$$p1) f(A, B, C, D) = \sum m(1, 3, 4, 5, 7, 8, 10, 13, 14, 15)$$


		Spajanje susjednih polja	
①	1v ①	1, 3 (2)	⑥) 1, 3, 5, 7 (2, 4) $\cancel{\cup}$ = 1, 3, 5, 7 (1, 4) = $\bar{A} \cdot D$
4v		1, 5 (4)	1, 5, 3, 7 (4, 2) $\cancel{\cup}$
8	4, 5 (1)	②) 5, 7, 13, 15 (2, 8) $\cancel{\cup}$	5, 7, 13, 15 (2, 8) $\cancel{\cup}$ = 5, 7, 13, 15 (2, 8) = B D
②	3v	8, 10 (2)	5, 10, 9, 15 (8, 2) $\cancel{\cup}$
5v	②) 3, 7 (4)	5, 7 (2)	5, 7 (2)
10			
③	7v	5, 13 (8)	
13		10, 14 (4)	
14	③) 7, 15 (8)		
④ 15		13, 15 (2)	
		14, 15 (1)	

Potpuna suma: {4, 5 (1); 8, 10 (2); 10, 14 (4); 14, 15 (1); 1, 3, 5, 7 (2, 4)}

{1, 7, 13, 15 (2, 8)} = {a, b, c, d, e, f}



1 3 4 5 7 8 10 13 14 15

1	✓													
2		✓												
3			✓											
4				✓										
5					✓									
6						✓								
7							✓							
8								✓						
9									✓					
10										✓				
11											✓			
12												✓		
13													✓	
14														✓
15														

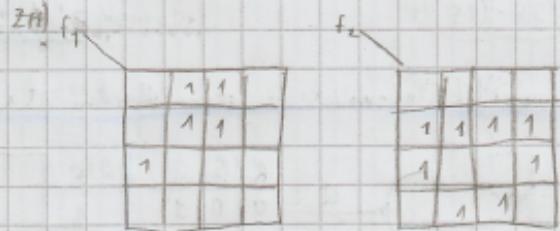

$$f = a + b + c + d + \{ \begin{matrix} c \\ d \end{matrix} \}$$
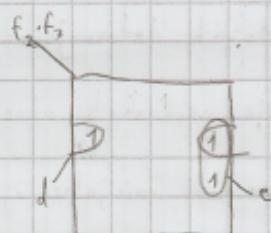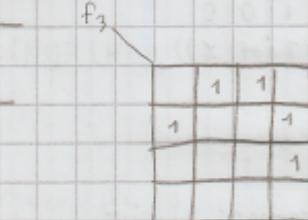
$$\begin{array}{c} 14 \\ \hline a & \checkmark \\ d & \checkmark \end{array}$$



Petrickov postupak

- u slučaju uvijek dvostrukog prekrivanja minterma

→ više od 1 kraćice u svakom stupcu

- minimalna suma = # prekrivanja

$$213) f = m_{38} + m_{42} + m_{46} + m_{50} + m_{54}$$

$$f = F(A, B, C, D, E, F)$$


$$38 = 32 + 4 + 2 = \underline{100} \underline{110} \quad \textcircled{3}$$

$$42 = 32 + 8 + 2 = \underline{10} \underline{10} \underline{10} \quad \textcircled{3}$$

$$46 = 32 + 8 + 4 + 2 = \underline{10} \underline{11} \underline{10} \quad \textcircled{3}$$

$$50 = 32 + 16 + 2 = \underline{11} \underline{00} \underline{10} \quad \textcircled{3}$$
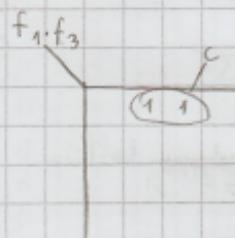
$$54 = 32 + 16 + 4 + 2 = \underline{11} \underline{01} \underline{10} \quad \textcircled{3}$$



$$f_1 = a + b + c$$

$$f_2 = b + d + e + a$$

$$f_3 = c + e + d$$

$$\begin{array}{l} \textcircled{3} \quad | \quad 38 & 38, 46(8) & a \\ | \quad 42 & 38, 54(16) & b \\ | \quad 50 & 42, 46(4) & c \\ \hline | \quad 50, 54(4) & d \end{array}$$


$$\begin{array}{l} \textcircled{4} \quad | \quad 46 \\ | \quad 54 \end{array}$$

	38	42	46	50	54
a	✓		✓		
b		✓		✓	
c					
d					

$$f = a + d + \{ \begin{matrix} a \\ b \end{matrix} \}$$

Bistabilni

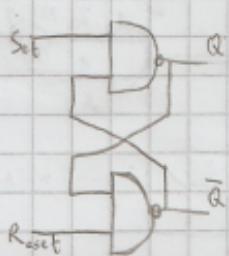- memorijski element u jednom od dva stanja



R	S	Q ⁿ⁺¹
0	0	0
0	1	1
1	0	0
1	1	X

$$Z17) f(a, b, c) = \sum m(0, 1, 5, 7)$$

$$= \overline{AB} + A\bar{C}$$

$$= (A+B)(\bar{A}+C)$$

A ₀	00	01	11	10
0	1	0	1	0
1	1	1	1	1

$$Z18) f(a, b, c) = \sum m(1, 3, 5, 7)$$

$$= \overline{AB} + AC$$

$$Z19) AD \begin{smallmatrix} 3 \\ -1 \\ 0 \\ 0 \end{smallmatrix} \begin{smallmatrix} 1 \\ 0 \\ 0 \\ 1 \end{smallmatrix} \begin{smallmatrix} 84 \\ 16 \\ 82 \\ 32 \end{smallmatrix}_{(10)} = \begin{smallmatrix} 2 \\ 37 \\ 530 \\ 528 \end{smallmatrix} \begin{smallmatrix} 305 \\ 7 \\ 949 \\ 092 \end{smallmatrix}_{(10)}$$

$$- \begin{smallmatrix} 16 \\ 82 \\ 60 \\ 33 \end{smallmatrix}_{(10)} = \begin{smallmatrix} 37 \\ 7 \\ 530 \\ 949 \end{smallmatrix}_{(10)}$$

$$FE FS FA 69_{(16)} = 2528 092 143_{(10)}$$

B-komplement

$$Z20) 1 \ 0000 \ 0000_{(2)} = 101 \ 0101_{(2)}$$

$$- \begin{smallmatrix} 1101 \\ 0101 \end{smallmatrix}_{(2)} = \begin{smallmatrix} 0010 \\ 1010 \end{smallmatrix}_{(2)}$$

$$0010 \ 1010_{(2)}$$

$$0010 \ 1011_{(2)}$$

AB	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	1	1	0	0
10	0	1	0	1

$$f = CD + BD + ACD + \overline{ACD}$$

$$= C(D + AD + \overline{AB}) + BD$$

$$= C(D + \overline{A}\overline{D}) + BD$$

$$Z21) f(A, B, C) = (B + \bar{C}) + (((B + C) \cdot C) + (B + \bar{A}))$$

$$f_D(A, B, C) = (B\bar{C}) \cdot (((B + C) + C) \cdot (B\bar{A}))$$

$$Z22) f = (\text{NOT}(\text{NOT } A \text{ OR } B) \text{ OR } B) \text{ OR } (B \text{ OR } C)$$

$$A \text{ OR } B = \text{NOR}(\text{NOR}(A, B))$$

$$= (\text{NOT}(\text{NOR}(\text{NOR}(\text{NOT } A, B) \text{ OR } B) \text{ OR } \text{NOR}(\text{NOR}(B, C)))$$

$$= (\text{NOT}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOT } A, B)), B) \text{ OR } \text{NOR}(\text{NOR}(B, C))))$$

$$\text{NOR}(\text{NOR}(B, C))$$

$$= \text{NOR}(\text{NOR}(\text{NOT}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOT } A, B),$$

$$, \text{NOR}(\text{NOR}(B, C))))$$

A ₀	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	1	1	0	0
10	0	1	0	1

$$Z23) f(A, B, C, D) = \overline{(CD + \overline{A}BD)} = (C + D) \cdot (A + \overline{B} + \overline{D})$$

$$= \overline{BD} + \overline{AD} + \overline{C}\overline{D} = (\overline{C} + D)(B + \overline{D})(\overline{A} + \overline{D})$$

$$=$$

$$\begin{aligned}
 f &= (\text{NOT}(\text{NOR}(\text{NOR}(\text{NOT } A, B))) \text{ OR } B) \text{ OR } (\text{NOR}(\text{NOR}(B, C))) \\
 &= \text{NOR}(\text{NOR}(\text{NOT}(\text{NOR}(\text{NOR}(\text{NOT } A, B)), B))) \text{ OR } (\text{NOR}(\text{NOR}(B, C))) \\
 &= \text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOT}(\text{NOR}(\text{NOR}(A \text{ NOR } A), B))), B))), \text{NOR}(\text{NOR}(B, C))) \\
 &= \text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}(\text{NOR}((A \text{ NOR } A), B))), B))), \text{NOR}(\text{NOR}(B, C)))
 \end{aligned}$$

21) 0010 1101 1110 1111 1111 0001 1101 010

0100 0100 0110 1110 0011 1111 1000 1111 0101 010

$$\begin{aligned}
 p_1 &= 3 \{0, 0, 0, 1, 0, 1, 1, 0, 1, 1, 1, 0, 1, 1, 0, 0, 0\} = 0 \\
 p_2 &= 12 \{0, 1, 0, 1, 0, 1, 0, 1, 1, 1, 1, 1, 1, 0, 1, 1, 1, 0\} = 1
 \end{aligned}$$

$$p_3 = \{110, 011, 1100, 010\} = 7 = 0$$

$$p_4 = \{011111, 01010\} = 9 = 0$$

$$p_5 = \{0, 1, 0, 1, 0\} = 2 = 1$$

$$\begin{aligned}
 25) \quad A &= 1000 \quad 1000 \quad 0111 \quad 0011 \quad 0000 \quad 0011 \\
 B &= 1100 \quad 0111 \quad 01100 \quad 0001 \quad 0010 \quad 0011
 \end{aligned}$$

Bistabilni

- Asinkroni

- Sinkroni (CP)

→ Bridi

- nastavci

- padajuci

→ Razina

- visoka

- niska

Naćini zapisivanja

- Tablica stanja

- Jednadjevom stanja $Q^{n+1} = f(Q^n, A^n)$




- Uzvodna tablica

- Dijagram stanja


→ čvor = stanje

→ strelica = prelaz

X	Y	Q^n	Q^{n+1}	$Q^{n+1} = f(X, Y, Q^n)$
0	0	0	0	$= \sum m(3, 4, 6, 7)$
0	0	1	0	
0	1	0	0	
0	1	1	1	
1	0	0	1	$Q^{n+1} = X \cdot \bar{Q}^n + Y \cdot Q^n$
1	0	1	0	
1	1	0	1	
1	1	1	1	

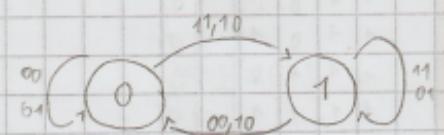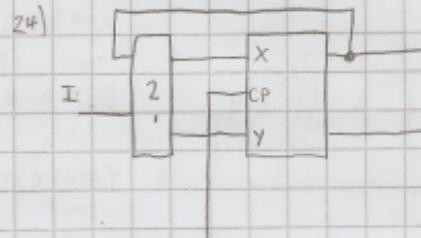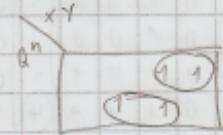


Q^n	Q^{n+1}	T	X Y	T	Q^n	X Y	$X = \sum m(2) + \sum d(1, 3)$
0	0	0	0 X	0	0	0 X	
0	1	1	1 X	0	1	X 1	$= f(T, Q^n)$
1	0	1	X 0	1	0	1 X	
1	1	0	X 1	1	1	X 0	$Y = \sum m(1) + \sum d(0, 2)$

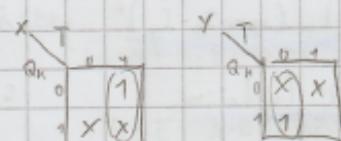

$$= f(T, Q^n)$$

X	Y	Q^n	J	K	Q^{n+1}	$Q^{n+1} = f(X, Y, Q^n) = \sum m(0, 3, 7, 9)$
0	0	0	0	0	0	\bar{Q}^{n+1}
0	0	1	0	0	1	\bar{Q}^{n+1}
0	1	0	0	0	0	\bar{Q}^{n+1}
0	1	1	0	0	1	\bar{Q}^{n+1}
1	0	0	1	0	1	\bar{Q}^{n+1}
1	0	1	0	0	1	\bar{Q}^{n+1}
1	1	0	1	0	1	\bar{Q}^{n+1}
1	1	1	1	0	0	$\bar{Q}^{n+1} = \bar{X} \cdot Q^n + X \cdot \bar{Q}^n + \bar{Y} \cdot Q^n$

23)

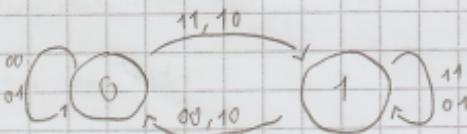

$$Q^{n+1} = \bar{X} \cdot Q^n + X \cdot \bar{Q}^n + \bar{Y} \cdot Q^n$$

Standardni kombinacijski mokuli

ostvaruju složenije široko korištene funkcije

- dekodiranje i kodiranje

- mapiranje koda nekoj vrijednosti

- n ulaza, 2^n izlaza

- potpuno : nepotpuno dekodiranje

- de koderi

- tipična funkcija: adresiranje

$$z) b_3 b_2 b_1 b_0 \quad \sum = f(b_3, b_2, b_1, b_0) \\ = \sum m(6, 8, 10)$$

0 0 0 0	0
0 0 0 1	0
0 0 1 0	0
0 0 1 1	0
0 1 0 0	2
0 1 0 1	0
0 1 1 1	4
0 1 1 0	5
1 0 0 1	6
1 0 0 0	0
1 0 1 1	3
1 0 1 0	0
1 1 0 1	0
1 1 0 0	0
1 1 1 1	0

=> multiplexer

- povezuje različite inpute i outpute

- tipična funkcija: vremenska raspodjelja

- osnova o bočnim ulazima (npr. \bar{A}, \bar{B}, C)

- dopušta prelaz inputa (npr. $I_0 - I_7$)

- korištenje trivijalnih funkcija

- za pojednostavljenje

- koristimo varijable najmanje

- težine (2^0) koja mogu biti onda

- ($C, \bar{C}, 0, 1$)

- prioritetski koder

- pokazuje da se promijenio ulaz

		D_0	D_1	D_2	D_3
		00	01	11	10
var min	0	1			
težine	1	1	1	1	1

$$D_0 = C$$

$$D_1 = 0$$

$$D_2 = C$$

$$D_3 = 1$$

$$b) C, 0, 1, C$$

$$z) f(A, B, C, D) = \sum m(2, 4, 6, 8, 9, 11)$$

		$A=0$	$A=1$
		0	1
0	1	1	1
1	0	1	1

$$D_0 = f(B, C, D) = B\bar{B} + C\bar{D} = \bar{D} * (B + C)$$

$$D_1 = f(B, C, D) = \bar{B}\bar{C} + \bar{B}D = \bar{B}(\bar{C} + D)$$

$$z) f(A, B, C), 2/1$$

$$D_0 = B + C$$

$$D_1 = B \oplus C$$

$$f = (B+C) \cdot \bar{A} + (B \oplus C) \cdot A$$

$$= \bar{A}B + \bar{A}C + A\bar{B}C + A\bar{B}\bar{C}$$

$$= \bar{A}B(C + \bar{C}) + \dots$$

$$= \sum m(1, 2, 3, 5, 6)$$

$$z) \bar{A}BE + ABC\bar{D} + DE\bar{F} + \bar{B}\bar{E}F, 4/1$$

6 varijabli, 4 ulaza sa svakom 4 varijable

$$a_1 = B, a_0 = E$$

$$d_1 = ?$$

$$d_0 = 1$$

VHDL

1.) Uključivanje biblioteka i paketa

2.) Definicija sučasnog sklopa (in & out)

3.) Definicija arhitekture sklopa

p1) $f \Leftarrow ((A \text{ and } B) \text{ or } C) \text{ and } D;$

$$= (AB + C) \cdot D$$

- Tip podataka std_logic (9)

- 0, 1, X (kratki spoj), U (undefined)

- Operatori:

- not $\rightarrow A \rightarrow \bar{A}$

A	A	\bar{A}
1	0	0
0	1	1
U	U	U

- and $\rightarrow A \wedge B \rightarrow A \cdot B$

A	0	1	U
B	0	0	0
0	0	0	0
1	0	1	U
U	0	U	U

- or $\rightarrow A \vee B \rightarrow A + B$

A	0	1	U
B	0	1	U
0	1	U	U
1	1	1	1
U	1	U	U

N1) $A \cdot \bar{A} \neq 0$

$$A \cdot \bar{A} = 0 \quad ;(;\; U)$$

- Komentari (- - bla bla)

- Implicitna lista osjetljivosti

- ulazi koji diktiraju vrijednost izlaza

- Ne razlikuje velika i mala slova

Aritmetički sklopori

$$24) 0 \text{ do } 3 \rightarrow 1 \text{ do } 4$$

• Zbrajala

$$4 \text{ do } 9 \rightarrow 6 \text{ do } 11$$

- potpuna

$$b_3 b_2 b_1 b_0 \text{ uLaz}$$

- nepotpuna

$$k_3 k_2 k_1 k_0 := \text{Laz}$$

• Oduzimala

b_3	b_2	b_1	b_0	k_3	k_2	k_1	k_0
0	0	0	1	0	1	0	1
1	0	0	1	0	1	0	0
2	0	0	1	1	2	1	0
3	0	1	0	0	3	1	0
4	0	1	1	0	4	0	1
5	0	1	1	1	5	0	1
6	1	0	0	0	6	0	1
7	1	0	0	1	7	0	0
8	1	0	1	0	8	0	0
9	1	0	1	1	9	0	0

3-komplement

Kodirano

- potpuna

- nepotpuna

• Prijenos (C_{in})

• Operacije se obavljaju bit po bit

b_3	b_2	b_1	b_0
00	00	01	10
X	X	(X)	1
01	X	X	
11	(1)	X	
10	(1)	X	

$$k_2 = \sum_u(6, 7, 8) + \sum_d(0, 5, 12, 13, 14, 15)$$

$$= b_3 \overline{b}_2 \overline{b}_0 + b_2 b_1$$

$$25) M = 5$$

$$N = 4$$

$$M \times N = 20$$

$$26) 0100001100100001 \rightarrow 5$$

$$= \begin{array}{r} 0 \quad 2 \quad 1 \quad 3 \\ 000000101000010001 \end{array}$$

$$= 0210 \{+6\}$$

$$27) Y_3 Y_2 Y_1 Y_0 = ?$$

$$b_3 b_2 b_1 b_0 = 1 \leftarrow 1 \leftarrow 0 \leftarrow 1$$

$$A_3 A_2 = 1 \ 0 = 2 \text{ paralel kružni}$$

$$1101 \rightarrow 1011 \rightarrow 0111$$

Sekvenčni sklopori

• Unutarnja memorija (registar)

• sinkronizacija sa CP



• dva klasična kanonska modela

- Mooreov automat

- Mealyjev automat

Mooreov automat

• izlaz ovisi samo o unutarnjem stanju

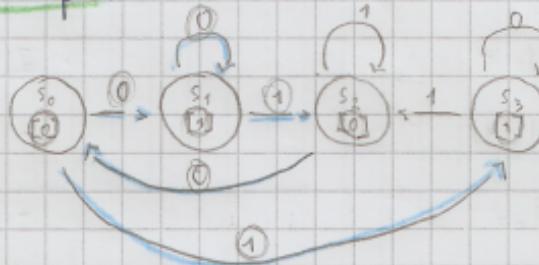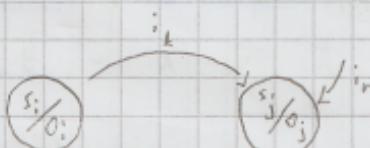

0, 1, 1, 0, 0, 1 s_3

Huffman-Mealyjeva metoda

1. podjela unutarnjih stanja u klase ekvivalentnih skupova

2. podjela na podklase

3. prelazi se zamjenjuju klasama

24) Ekvivalentna stanja = ?

Mealyjev automat

• izlaz ovisi o unutarnjem stanju i ulazu

	Stanje	Pobuda	Slijedeće stanje	Izlaz
21)	s_3	0	s_2	0
		1	s_4	0
	s_7	0	s_2	1
		1	s_4	1

- Stanja nisu ekvivalentna jer imaju različite izlaze

$s_1 \vdash s_3$

Q^n	Q^{n+1}	Z_n
s_0	0 1	
s_1	$s_1 \quad s_3$	0
s_2	$s_1 \quad s_2$	1
s_3	$s_3 \quad s_2$	0
	$s_3 \quad s_2$	1

1. Klasa

	a	b
Stanje	$s_0 \quad s_2 \quad s_1 \quad s_3$	
Slijedeća klasa	b b a a b a b a	

2. Klasa

	a	b	c
Stanje	$s_0 \quad s_1 \quad s_3 \quad s_2$		
Slijedeća klasa	b b b c b c a c		

22) Bistabilni B_0, B_1, B_2

- Izlazi Q_0, Q_1, Q_2

Izlaz Mooreovog troja $Z = ?$

Uzlaz: X, Y

Z može biti: $Q_1 \oplus Q_0 + Q_2$

25) Broj parova ekvivalentnih stanja = ?

$s_1 \equiv s_2$

23) Mooreov automat

Broj parova = 1

Početno stanje je s_0

Dovodi se niz na ulaz: 0, 0, 1, 0, 1

Izlaz, stanje = ?

Ostvarivanje sekvenčnih sklopova

• D, T i JK bistabilima


- $D_n = B^{n+1}$

26) Dva JK bistabila

I_1, I_2 i B_1, B_0 učinkom: Q_1, Q_0

Ulavac strojna: I

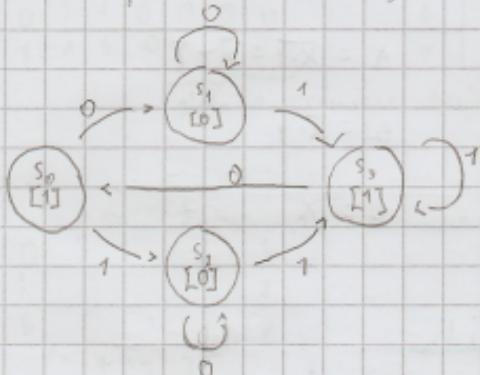Minimalni zapis booleane funkcije $D_1 = ?$



Q^n	Q^{n+1}		$(Q_1, Q_0)^{n+1}$	
	$I=0$	$I=1$	$I=0$	$I=1$
S_0	S_1	S_2	00	01 10
S_1	S_2	S_3	01	01 11
S_2	S_3	S_1	10	10 11
S_3	S_0	S_1	11	00 11

$(Q_1, Q_0)^n$	Q_1^{n+1}		Q_0^{n+1}	
	$I=0$	$I=1$	$I=0$	$I=1$
00	0	1		
01	0	1	00 01 11 10	
10	1	1		
11	0	1		

$(Q_1, Q_0)^n$	Q_0^{n+1}	
	$I=0$	$I=1$
00	1	0
01	1	1
10	0	1
11	0	1


Q^n	Q^{n+1}		Z^n	(B_1, B_0)	$(B_1, B_0)^{n+1}$		Z^n
	$A=0$	$A=1$			$A=0$	$A=1$	
S_0	S_1	S_2	0		00	01 11	0
S_1	S_2	S_3	1		01	01 10	1
S_2	S_3	S_1	0		10	00 10	0
S_3	S_1	S_2	1		11	11 10	1

$$B_1^{n+1} = f_1(B_1^n, B_0^n, A)$$

$$B_0^{n+1} = f_0(B_1^n, B_0^n, A)$$

A	00	01	11	10
00	00	01	10	01
01	11	11	11	11
11	11	11	11	11

1 promjena stanja

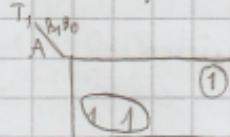

$$T_1 = \overline{B_1} \cdot A + B_1 \overline{B_0} \cdot \overline{A}$$

$$T_0 = \overline{B_1} \overline{B_0} + B_0 A$$

- 28) Dva JK bistabila

- postupak isti:

Vremenski odnosi:

* max frekvencija rada bistabila (f_{max})

$$D_1 = Q_1^{n+1} = \overline{Q}_1 \overline{I} + Q_1 \cdot I + \overline{Q}_1 Q_0$$

$$= \overline{Q}_1 \cdot \overline{I} + \overline{Q}_1 \cdot I + Q_0 \cdot I$$

* vrijeme kašnjenja (t_d)

* vrijeme postavljanja (t_{setup})

* vrijeme otpuštanja ($t_{release}$)

* vrijeme pridržavanja (t_{hold})

29) Dva T bistabila

$$- 29) t_{HLS} = 10 \text{ ns}$$

$$T_{min} = t_{db} + t_{dl} + t_{setup} = 50 \text{ ns}$$

$C_i \rightarrow :$

$$t_{hold} = 10 \text{ ns}$$


$$f_{max} = \frac{1}{T_{min}} = \frac{1}{50 \text{ ns}} = 20 \text{ MHz}$$

$$t_{setup} = 10 \text{ ns}$$

$$t_{db} = 30 \text{ ns}$$

$$f_{max} = ?$$

$T_1 = ?$

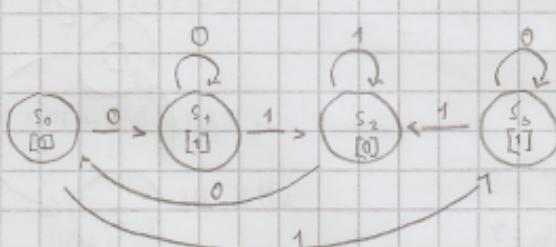

- Standardni sekvencijski moduli -

- sadrže kombinacijski sloop i memoriju

• registri

- registri u užem smislu

- posnačni registri

• brojila

- sinkrona brojila

- asinkrona brojila

- brojila na temelju posnačnog registra

A	B	S_{in}	X	Y	posnak	S_{in}
0	0	Q_3	0	0	L	S_{in}
0	1	Q_2	0	1	L	1
1	0	S_{in}	1	0	D	S_{in}
1	1	1	1	1	D	Q_3

X	Y	C	S_{in}	A	B
0	0	0	d_4	1	0
0	1	0	d_3	1	1
1	0	1	d_2	1	0
1	1	1	d_1	0	0

$$A = \overline{X} \cdot Y = \overline{X} + \overline{Y}$$

$$B = \overline{X} \cdot Y$$

$$C = X$$

Brojila

• Brojila u užem smislu

- važan je redoslijed izmjenе stanja

• Digitalne frekvencije

- važno samo okretena stanja

- pojednostavljeni dekoder

• Sinkrona brojila (t_{setup})

- binarna brojila

- Brojila modulo $m \neq 2^n$ (izguran stanje)

- prijenos


$$\rightarrow \text{Paralelan } f_{\max} = \frac{1}{t_{\text{setup}} + t_{\text{db}} + t_{\text{dI}}}$$

- Brzijalivije AND sklopova

$$\rightarrow \text{Serijski } f_{\max} = \frac{1}{t_{\text{setup}} + t_{\text{db}} + t_{\text{dI}}}$$

- Kaskadiranje AND sklopova

\rightarrow Sporijalni jeftiniji:

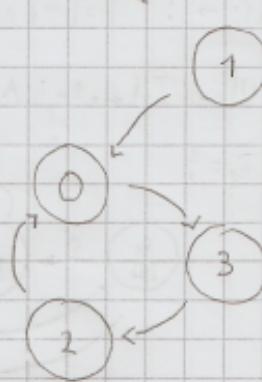

$C=0 \rightarrow$ posnak podatka u lijevo

$C=1 \rightarrow$ posnak podatka u desno

Unos u vijeće S_{in}/Y

Premjena upravljačkih ulaza u $X : Y$

$XY=00 \rightarrow$ posnak u lijevo (S_{in})

$XY=01 \rightarrow$ posnak u lijevo (1)

$XY=10 \rightarrow$ posnak u desno (S_{in})

$XY=11 \rightarrow$ posnak u desno (Q_3)

22) Ciklus brojila = 8

$$A = ?$$

$$T_2 = Q_1 + Q_0$$

$$T_1 = \overline{Q}_2 + \overline{Q}_0$$

$$J_0 = K_0 = T_0 = \overline{Q}_2 \cdot Q_1$$

Programirajivi moduli

* ostvarivanje složnije funkcije koja nije unaprijed adresirana (programiranje)

* osnovna struktura je dekoder-koder

* oblici:

- permanentna memorija: ROM

- jednostrukni PLD (SPLD): PLA, PAL

- složeni PLD (CPLD)

→ više povezanih SPLD-a

- programirljiv polje logičkih blokova: FPGA

→ vrlo složeni PLD karakteristične strukture

z2) Očitanje $\{0, 1, 2, 3, 3, 2, 1, 0; 0, 1, 1, 3, 2, 2, 2, 1\}$

i	i_3	i_2	i_1	i_0	PG	m_1	m_0	d_2	d_1	d_0	Ulaž
0	0	0	0	0	0	0	0	0	0	0	000
1	0	0	0	1	1	1	0	1	0	1	113
2	0	1	0	1	0	2	1	0	1	0	115
3	0	0	1	1	3	1	1	1	1	1	1F
4	0	1	0	0	3	1	1	1	1	1	1F
5	0	1	0	1	2	1	0	1	1	0	0C
6	0	1	1	0	1	0	1	0	1	0	0A
7	0	1	1	1	0	0	0	0	0	1	111
8	1	0	0	0	0	0	0	0	0	0	000
9	1	0	0	1	1	0	1	0	1	0	111
A	1	0	1	0	1	0	1	0	1	0	111
B	1	0	1	1	3	1	1	1	1	0	111
C	1	1	0	0	3	1	1	0	1	1	111
D	1	1	0	1	2	1	0	1	1	0	110
E	1	1	1	0	2	1	0	1	1	0	110
F	1	1	1	1	1	1	0	1	1	1	111

ROM


* dekoder obavlja potpuno binarna dekodiranje

* dekodersko / I polje

* kodersko / LILI polje

* LUT (lookup table)
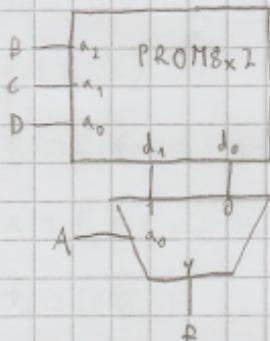
$$z1) f = \sum m(0, 1, 3, 5, 8, 12, 13, 15)$$



$$8 \times 2 = 16 \quad \checkmark \text{ (možuće ostvariti funkciju)}$$

ROM (MUX)

Očitanje ROM-a: 0101 12302

	$a_0 = A$	B	C	D	d_1	d_0
0	0	0	0	1	1	3
0	0	0	1	0	1	1
0	0	1	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	0	2
1	0	0	1	1	1	2
1	1	0	0	0	0	0
1	1	1	1	0	2	2

PLA


* veća efikasnost (nepotpuno specifikovane funkcije)

* ulazi primarni implikanti (minimizacija)

* proširivanje funkcionalnosti;

- dodavanje XOR s ulazom za upravljanje
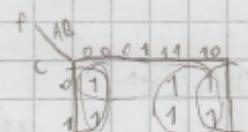
$$z3) f = \bar{A} \bar{B} \bar{C} + A C + A \bar{B} \bar{C} + \bar{A} \bar{B} C + A \bar{B} \bar{C}$$



$$f = A + \bar{B}$$

$$z4) \bar{f}_1 = \overline{x_2 + \bar{x}_1} + \overline{\bar{x}_2 + \bar{x}_0} + \overline{x_1 + \bar{x}_0}$$

$$\bar{f}_2 = \overline{x_2 + \bar{x}_1} + \overline{\bar{x}_2 + x_0}$$

$$f_1 = (x_2 + \bar{x}_1) \cdot (\bar{x}_2 + \bar{x}_0) \cdot (x_1 + \bar{x}_0)$$

$$f_2 = (x_2 + \bar{x}_1) \cdot (\bar{x}_2 + x_0)$$

x_2	x_1	x_0	f_1
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

x_2	x_1	x_0	f_2
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$f_1 = x_2 \cdot \bar{x}_0 + \bar{x}_1 \cdot \bar{x}_0$$

$$f_2 = \bar{x}_2 \cdot \bar{x}_1 + x_2 \cdot x_0$$


$$z_5) f = \overline{A+C} + \overline{A+C} + \overline{B+C}$$

$$Q_2^{n+1} = \sum m(0, 2, 5, 6) = S_{in}$$

$$f = (\bar{A}+C)(\bar{A}+\bar{C})(B+C)$$

$$g = \overline{B+D} + \overline{B+C} + \overline{B+D}$$

$$g = (B+\bar{D})(B+C)(B+\bar{D})$$

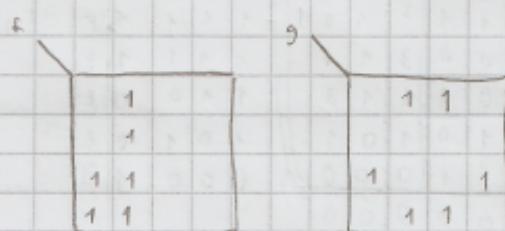

$$f = \overline{AB} + \overline{AC}$$

$$g = \overline{BD} + \overline{BC}D$$

		n+1			
		Q ₀	Q ₁	Q ₂	Q ₃
		00	01	11	10
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	0	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	1	1	0	0
1	1	0	1	1	1
1	1	0	1	0	1

$$Q_2^{n+1} = Q_2 \overline{Q}_1 Q_0 + \overline{Q}_2 \overline{Q}_0 + Q_1 \overline{Q}_0$$

$3 \times 3 \times 1$

• PLA

- poluprogramirljive logičke polje
- samo dekoder

$$z_6) f = \overline{(A+C)} + (\bar{A}+\bar{C})$$

$$f = (A+C)(\bar{A}+\bar{C})$$

$$f = A \oplus C$$

$$\overline{f} = \overline{B+\bar{F}} + \overline{B+\bar{B}} + \overline{B+F}$$

$$f = (\bar{B}+\bar{F})(B+F)$$

$$f = B \oplus F$$

$$f = A \oplus B \oplus C \rightarrow \text{šahovska ploča}$$

f

AB		C			
		00	01	11	10
		0	1	1	1
		1	1	1	1

$$f(A, B, C) = \sum m(1, 2, 4, 7)$$

$$z_8) f = \prod M(0, 1, 4, 5, 13, 15)$$

$$f_2 = \prod M(0, 1, 4, 5, 7, 15)$$

2 funkcije $m \times n \times 2$

4 ulaza $4 \times n \times 2$

f ₁		f ₂	
A+C	$\bar{A}\bar{B}$	A+C	$\bar{B}\bar{C}\bar{D}$
1	1	1	1
1	1	1	1

$4 \times 4 \times 2$

$$z_7) \text{Ciklus: } 0, 1, 4, 2, 5, 6, 7, 3, 1$$

$$Q_2 \rightarrow Q_1 \rightarrow Q_0 \text{ cmjer}$$

$$S_{in} = ?$$

3 varijable ($2^3 = 8$) $3 \times n \times m$

1 ulaz $3 \times n \times 1$

n	n+1
Q ₀	Q ₁ Q ₀
0	0 0
0	0 1
0	1 0
0	1 1
1	0 0
1	0 1
1	1 0
1	1 1

$$f = X_2 + (1 + \bar{X}_1) + X_1 \cdot \bar{X}_0$$

$$f = X_2 + X_1 \cdot \bar{X}_0$$

$$f = X_2 + X_1 \cdot \bar{X}_0$$

$$f = X_2 + X_1 \cdot \bar{X}_0$$

FPGA

• dvodimenzionalno polje logičkih blokova

- kombinacijsko i sekvenčno ponašanje

$$z13) X_2 = A$$

$$x_1 = B$$

$$x_0 = C$$

$$Q^{n+1} = \bar{A} \cdot \bar{Q}_n + B$$

$$LUT = ?$$

x_2	x_1	x_0	A	B	Q_n	Q^{n+1}	Z
0	0	0	1	0	0	1	1
0	0	1	0	1	0	0	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	1	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	1	0	1
1	1	1	0	0	0	1	1

$$z10) f = A \cdot (B \oplus C)$$

$$LUT = ?$$

A	B	C	$B \oplus C$	$A \cdot (B \oplus C)$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

$$LUT = 0, 0, 0, 0, 0, 1, 1, 0$$

$$z11) P_0 = \overline{A \cdot B}$$

$$P_1 = C \cdot D$$

$$f = P_0 \oplus P_1$$

$$f = (\overline{A \cdot B}) \oplus (C \cdot D)$$

$$z12) f = A + (B \equiv C) = A + (\overline{B \oplus C})$$

$$LUT_1 = ?$$

$$P_0 = B \oplus C$$

$$P_1(f_0, C) = ?$$

$$P_2 = \overline{A \cdot P_1} = f = A + \overline{P_1}$$

$$A + \overline{P_1} = A + (\overline{B \oplus C})$$

$$\overline{P_1} = \overline{(B \oplus C)}$$

$$P_1 = B \oplus C = P_0$$

a_1	a_0	y
0	0	0
0	1	0
1	0	1
1	1	1

$$LUT_1 = 0, 0, 1, 1$$

$$z14) Q^{n+1} = Q_n \cdot B + A \bar{D}$$

$$LUT, S = ?$$

$S = 1 \rightarrow$ sklop bude sekvenčni

a_2	a_1	a_0	A	B	Q^n	Q^{n+1}	Z
0	0	0	0	0	0	0	d_0
0	0	1	0	1	0	1	d_1
0	1	0	0	0	0	0	d_2
0	1	1	1	1	1	1	d_3
1	0	0	1	0	1	1	d_4
1	0	1	1	1	1	1	d_5
1	1	0	0	0	0	0	d_6
1	1	1	1	1	1	1	d_7

$$LUT = 0, 0, 0, 1, 1, 1, 0, 1$$

$$z15) Ciklički: sljed : 3, 7, 2, 1$$

$s = 0 \rightarrow$ sklop je kombinacijski

$s = 1 \rightarrow$ sklop je sekvenčni

$$LUT_4 = ?$$

b_1	b_2	n	$n+1$
$b_1 = a_1$	$b_2 = a_0$	b_1	b_2
0	0	0	0
1	0	1	0
2	1	0	1
3	1	1	0

b_1	b_2	0_1	0_0
0	0	0	1
1	0	1	1
2	1	0	0
3	1	0	1

$$LUT_4 = 1, 1, 1, 0$$

Svečanje s analognom okolinom

• upravljanje prikupljanjem podataka iz

$$V_{t=50\mu m} = -1.25 V$$

stvarnog svijeta (senzori) - ADC

$$V_{t=150\mu m} = -2.5 V$$

• vraćanje rezultata u stvarni svijet

$$V_{t=250\mu m} = -3.75 V \rightarrow 2200 \mu m$$

putem aktivatora - DAC

$$U_{out} = -2.5 V$$

• ulaz: pretvorba (analognog) napona u broj (A/D)

z3) 6-bitni DAC za kod 222111

• izlaz: pretvorba broja u (analogni) napon

$$U_{REF} = 5 V$$

• parametri pretvorbe

$$U_{out14} = ?$$

$$\text{- rezolucija: } \frac{U_k}{U_H} = \frac{1}{n_H} = \frac{1}{2k-1}$$

$$U_{out1} = - \frac{U_{REF}}{R_{ckv}} = - \frac{U_{out}}{R_f}$$

$$\text{- tačnost (granica pogreške): } \epsilon_i = \frac{\Delta U}{U_H}, \epsilon_d \frac{\Delta U_k}{U_k}$$

$$R_f = -R_{ckv} \cdot \frac{U_{out}}{U_{REF}}$$

• vrijeme pretvorbe

$$"7" = 111001 \rightarrow \frac{1}{R_{ckv}12} = 3 \cdot \frac{1}{1102} + \frac{1}{2102} = \frac{7}{2} \text{ ms}$$

z1) 4-bitni D/A

$$R_{ckv12} = \frac{2}{7} k\Omega$$

$$R_1 = 8 k\Omega \rightarrow R_2 = 4 k\Omega, R_4 = 2 k\Omega, R_8 = 1 k\Omega$$

$$R_f = \frac{2}{7} \cdot \frac{10}{5} = \frac{4}{7} k\Omega = 571 \Omega$$

$$4_{10} = 0100_2 \text{ je } R_{ckv} = R_4$$

$$"4" = 011000 \rightarrow R_{ckv14} = 0.5 k\Omega$$

$$\frac{U_{REF}}{R_{ckv}} = - \frac{U_{out}}{R_f}$$

$$U_{out14} = -U_{REF} \cdot \frac{R_f}{R_{ckv14}} = -5 \cdot \frac{4}{7} \cdot 2 = -40 = -5.71 V$$

$$U_{out} = -5 \cdot \frac{4}{2} = -10 V$$

z4) 14 bitova \rightarrow 13 bitova

2 puta manjom rezolucijom

z2) $t_P = 500 \mu s \rightarrow T = 1 \text{ ms}$

2 puta veća pogreška (za 100%)

$$t = 2.2 \text{ ms} = 2200 \mu s$$

$$R = 1 k\Omega$$

$$R_f = 2 k\Omega$$

$$0 \rightarrow 0V, 1 \rightarrow +5V$$

$$U_{out} = U_{REF} \cdot \frac{R_f}{R_1} = -5 \cdot \frac{2}{8 \cdot 1} = -1.25 V$$

Implementacija log. sklopova

- CMOS tehnologija - današnji izbor

$$\Sigma 1) \overline{A+B} \cdot C = f$$

- problemni ekvi. prikaz log. vrijednosti:

$$f = \overline{A} \cdot \overline{B} \cdot C$$

- smetnje

$$= m_7$$

- opterećenje

$$= \prod (0, 2, 3, 4, 5, 6, 7)$$


- međuovisnost dissipacije snage i brzine

- funkcije N1 ; NIL1

- implementacija

- N1 - serijski spoj sklopki

- osnovne funkcije (I ; ILI)

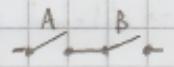

- komplementiranje (NE)

- NIL1 -> paralelan spoj sklopki

- funkcije N1 ; NIL1

CMOS tehnologija

- > kombinacija invertora i osnovnih funkcija

- kombinacija NMOS ; PMOS tranzistora

- > direktno povezivanje tranzistora (MOSFET)

- NMOS radi na visoku razinu

- vrste logike

- PMOS radi na nisku razinu

- pozitivna ($1 \sim V$, $0 \sim N$)

- inverter -> kombinacija NMOS ; PMOS

- negativna ($0 \sim V$, $1 \sim N$)


21)		
A	B	f
-2V	-2V	-4V
-2V	-4V	-4V
-4V	-2V	-4V
-4V	-4V	-2V

$f = ?$ negativna logika
 \downarrow
 $-2V \sim 0, -4 \sim 1$

A	B	f
0	0	1
0	1	1
1	0	1
1	1	0

$f = N1$

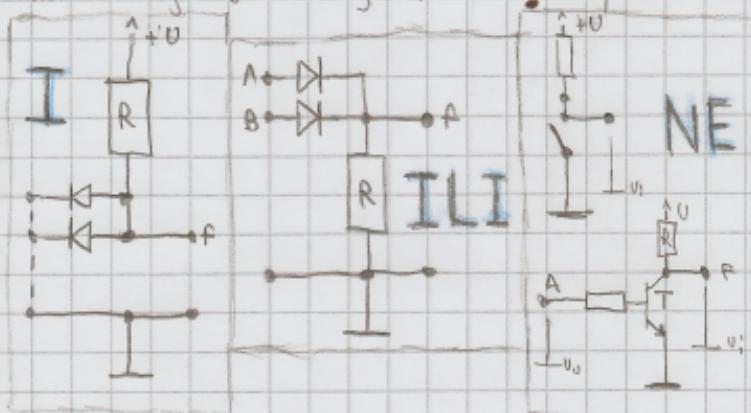- Osnovne logičke funkcije / i inverter (prikaz)



Memorijski moduli

• memorija

- digitalni (pod)sustav za pamćenje
većeg broja podataka

- struktura:

→ memorijска polje (skup celija)

→ sklopovi za pristup (dekoder)

→ sklopovi za čitanje i pisanje

- pristup: serijski i paralelni

Dinamičke memorije (DRAM)

Z) Nakon 26 impulsa CP, upis 01101001

F3 47 35 01₁₆ = 1111 00111 01000111 00110101 00000001₂
 ↓ ↓
 A7 47 35 01₁₆ = 10100111 000011 00110101 00000001₂

Statičke memorije (SRAM)

• volatilne (nepostojana)

• tehnologije: bipolarna (cache) : MOSFET (RAM)

• organizacija

- dekoder

- memorijска polje

- međusklop (čitanje i pisanje)

• organizacija mem. polja

- 2D (dekoder 2^n)

- 3D (2 dekodera $2^n/2$)

- 2.5D

→ poboljšano 2D (podjela na podpolja)

→ manji broj nijeći s većim brojem bitova

→ npr. iz 256×1 u 64×4

• projektiranje memorije (povezivanje polja)

- dodavanje dekodera za pristup polju